

Example:

Consider a transistor with the following S-parameters (common emitter):

$$S_{11}^E = 0.33 \angle 85^\circ \quad S_{12}^E = 0.34 \angle 56^\circ$$

$$S_{21}^E = 1.39 \angle 39.6^\circ \quad S_{22}^E = 0.26 \angle -47^\circ$$

3-port S-parameters

$$S = \begin{bmatrix} 0.50 \angle -84^\circ & 0.49 \angle 39.6^\circ & 0.60 \angle 17.8^\circ \\ 1.31 \angle 45.4^\circ & 0.39 \angle -69.7^\circ & 0.56 \angle -95.3^\circ \\ 0.43 \angle -85.8^\circ & 0.49 \angle 6.12^\circ & 0.61 \angle 38.2^\circ \end{bmatrix}$$


I am going to put the load off the emitter. So, I want to first pick Γ_1 to maximize $|S_{33}^T|$

$$S_{33}^T = S_{33} + \frac{S_{31} S_{13} \Gamma_1}{1 - S_{11} \Gamma_1} = \frac{S_{33} - \Delta_3 \Gamma_1}{1 - S_{11} \Gamma_1} \quad \text{where } \Delta_3 = S_{11} S_{33} - S_{31} S_{13}$$

$$\Gamma_1 = \frac{S_{33} - S_{33}^T}{\Delta_3 - S_{11} S_{33}^T}$$

$$C_1 = \frac{S_{33} - \Delta_3 S_{33}^T}{1 - |S_{11}|^2} = 0.76 \angle 68^\circ$$

$$\Gamma_1 = \left| \frac{S_{13} S_{31}}{1 - |S_{11}|^2} \right| = 0.60$$

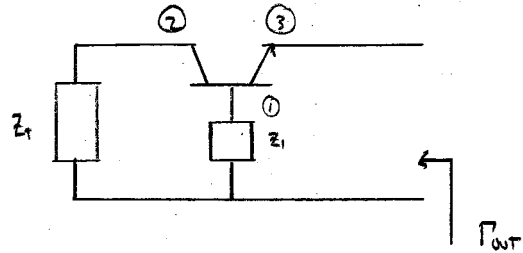

$$S_{33}^T, \max = (0.76 + 0.60) \angle 68^\circ = 1.36 \angle 68^\circ$$

$$\Gamma_1 = 1 \angle 144^\circ$$

Use value of Γ_1 to compute $S_{22}^T, S_{13}^T, S_{32}^T, S_{33}^T$

$$P_{out} = S_{33}^T + \frac{S_{32}^T S_{23}^T \Gamma_T}{1 - S_{22}^T \Gamma_T} = \frac{S_{33}^T - \Delta^T \Gamma_T}{1 - S_{22}^T \Gamma_T} \quad \Delta^T = S_{33}^T S_{22}^T - S_{23}^T S_{32}^T$$

$$\Gamma_T = \frac{S_{33}^T - P_{out}}{\Delta^T - S_{22}^T P_{out}}$$

$$C_{out} = \frac{S_{33}^T - \Delta^T S_{22}^{T*}}{1 - |S_{22}^T|^2} = 2.56 \angle 46^\circ$$

$$\Gamma_{out} = \left| \frac{S_{23}^T S_{32}^T}{1 - |S_{22}^T|^2} \right| = 1.75$$

$$P_{out, \max} = (2.56 + 1.75) \angle 46^\circ$$

$$\Gamma_T = 1 \angle 112^\circ$$

$$Z_{out} = -64.5 + j22.8 \Omega$$