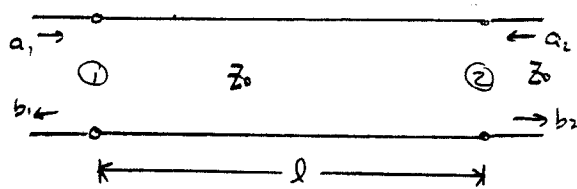


4.10 Derive the S-matrix for each of the following networks, relative to a system impedance of Z_0 .



Since the line is of impedance Z_0 , if we terminate port 2 in Z_0 , $S_{11} = 0$. Similarly, $S_{22} = 0$.

On the line: $V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z} = V^+ e^{-j\beta z}$ since $V^- = 0$ (no reflections due to match)

Since $S_{11} = 0$, $b_1 = 0$

Also, $a_2 = 0$.

$$\sqrt{Z_0} a_1 = V(-l) = V^+ e^{j\beta l}$$

$$\sqrt{Z_0} b_2 = V(0) = V^+$$

$$\frac{b_2}{a_1} = \frac{1}{e^{j\beta l}} = e^{-j\beta l}$$


$$S = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$

Obviously:

$$|S_{11}|^2 + |S_{21}|^2 = 0 + 1 = 1$$

$$|S_{12}|^2 + |S_{22}|^2 = 1$$
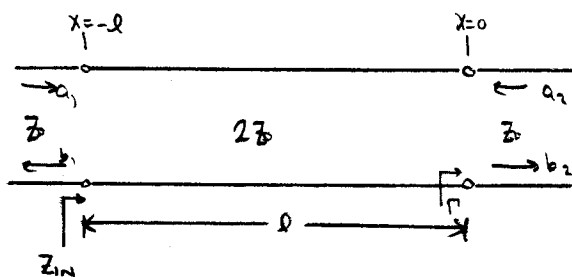
$$S_{11} S_{21}^* + S_{21} S_{11}^* = 0$$



If we terminate port ② in Z_0

$$Z_{in} = Z_0 \frac{Z_0 + jZ_0 \tan \beta l}{Z_0 + jZ_0 \tan \beta l} = Z_0 \frac{1 + j2 \tan \beta l}{2 + j \tan \beta l}$$

$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z_0(1 + j2 \tan \beta l) - Z_0(2 + j \tan \beta l)}{Z_0(1 + j2 \tan \beta l) + Z_0(2 + j \tan \beta l)} = \frac{j3Z_0 \tan \beta l}{4Z_0 + j5Z_0 \tan \beta l} = \frac{3}{5 - j4 \cot \beta l}$$

On the line: $V(x) = V^+ e^{-j\beta x} + \Gamma e^{j\beta x} = V^+ [e^{-j\beta x} + \Gamma e^{j\beta x}]$

$$\Gamma = \frac{Z_0 - Z_{in}}{Z_0 + Z_{in}} = -\frac{1}{3}$$

$$V(x) = V^+ [e^{-j\beta x} - \frac{1}{3} e^{j\beta x}]$$

Equality of voltages at $x=0$ and $-l$

$$V(0) = V^+ [1 - \frac{1}{3}] = \sqrt{Z_0} (a_2 + b_2)$$

$$(E1) \quad \frac{2}{3} V^+ = \sqrt{Z_0} b_2 \quad (\text{since } a_2 = 0 \text{ when port ② is terminated in } Z_0)$$

$$V(-\omega) = V^+ [e^{j\beta l} - \frac{1}{3} e^{-j\beta l}] = \sqrt{3} (a_1 + b_1)$$

$$(E2) \quad V^+ [e^{j\beta l} - \frac{1}{3} e^{-j\beta l}] = \sqrt{3} a_1 (1 + S_{11})$$

Taking the ratio of (E1) and (E2):

$$\frac{\sqrt{3} b_2}{\sqrt{3} a_1 (1 + S_{11})} = \frac{\frac{2}{3} V^+}{V^+ [e^{j\beta l} - \frac{1}{3} e^{-j\beta l}]}$$

$$S_{21} = \frac{b_2}{a_1} = \frac{2(1 + S_{11})}{3(e^{j\beta l} - \frac{1}{3} e^{-j\beta l})}$$

$$S_{11} = S_{22} = \frac{3}{5 - j4 \cot \beta l}$$

$$S_{21} = S_{12} = \frac{2(1 + S_{11})}{3(e^{j\beta l} - \frac{1}{3} e^{-j\beta l})}$$

4.16

$$S = \begin{bmatrix} 0.1 \angle 90^\circ & 0.8 \angle -45^\circ & 0.3 \angle 45^\circ & 0 \\ 0.8 \angle -45^\circ & 0 & 0 & 0.4 \angle 45^\circ \\ 0.3 \angle -45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.4 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}$$

(a) Is this network lossless?

$$\text{Try: } |S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 = 0.1^2 + 0.8^2 + 0.3^2 + 0 = 0.74 \neq 1$$

No.

(b) Is this network reciprocal?

$$\text{Since } S = S^T$$

Yes

(c) What is the return loss at port 1 when all other ports are matched?

$$\text{With all ports matched: } RL = -20 \log |S_{11}| = -20 \text{ dB}$$

4.16(d) What is the insertion loss and phase between ports 2 and 4, when all other ports are matched?

$$IL = -20 \log |S_{42}| = -20 \log 0.4 \Rightarrow IL = 7.96 \text{ dB}$$

$$\text{Insertion Phase} = \angle S_{42} = 45^\circ$$

(e) What is the reflection coefficient at port 1 if port 3 is shorted and all other ports are matched?

$$a_2 = a_4 = 0$$

$$a_3 = -b_3$$

$$b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3 + S_{14}a_4 = S_{11}a_1 - S_{13}b_3 \quad (E1)$$


$$b_3 = S_{31}a_1 + S_{32}a_2 + S_{33}a_3 + S_{34}a_4 = S_{31}a_1 - S_{33}b_3 \quad (E2)$$

$$\text{Solving (E2): } b_3 = \frac{S_{31}}{1 + S_{33}} a_1$$

$$\text{Placing this into (E1): } b_1 = S_{11}a_1 - \frac{S_{13}S_{31}}{1 + S_{33}} a_1$$

$$\Gamma_1 = \frac{b_1}{a_1} = S_{11} - \frac{S_{13}S_{31}}{1 + S_{33}} \quad 0.1 \angle 90^\circ - 0.3 \angle -90^\circ = j(0.1 + 0.3) = 0.4 \angle 90^\circ$$

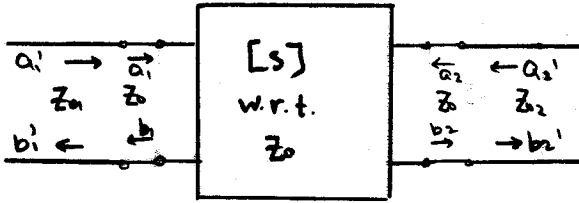A two port has S-parameters S_{ij} for a system impedance of Z_0 . Find the new S parameters for the network shown.



Assume an infinitesimal length of line (Z_0) attached to the end of the 2-port.

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

If we terminate port ② with Z_2 ($a_2 = 0$)

$$\Gamma_2 = \frac{Z_2 - Z_0}{Z_2 + Z_0}, \quad a_2 = \Gamma_2 b_2$$

$$b_2 = S_{21} a_1 + S_{22} \Gamma_2 b_2 \quad (\text{from 2nd line of matrix})$$

$$b_2 = \frac{S_{21} a_1}{1 - S_{22} \Gamma_2}$$

$$b_1 = S_{11} a_1 + S_{12} \Gamma_2 b_2 \quad (\text{from 1st line of matrix})$$

$$= S_{11} a_1 + \frac{S_{12} \Gamma_2 S_{21} a_1}{1 - S_{22} \Gamma_2} = \left[S_{11} + \frac{S_{12} S_{21} \Gamma_2}{1 - S_{22} \Gamma_2} \right] a_1$$

$$\text{So, } \frac{b_1}{a_1} = \frac{S_{11} + \frac{S_{12} S_{21} \Gamma_2}{1 - S_{22} \Gamma_2}}{1} = \Gamma_{11} \text{ is the reflection coefficient with respect to } Z_0.$$

We need to compute the reflection coefficient with respect to Z_{11} .

$$Z_{11} = Z_0 \frac{(1 + \Gamma_{11})}{(1 - \Gamma_{11})}$$

$$S_{11}' = \frac{Z_{11} - Z_0}{Z_{11} + Z_0} = \frac{Z_0 (1 + \Gamma_{11}) - Z_0 (1 - \Gamma_{11})}{Z_0 (1 + \Gamma_{11}) + Z_0 (1 - \Gamma_{11})}$$

$$S_{11}' = \frac{Z_0 (1 + \Gamma_{11}) - Z_0 (1 - \Gamma_{11})}{Z_0 (1 + \Gamma_{11}) + Z_0 (1 - \Gamma_{11})} \quad \text{where } \Gamma_{11} = \frac{S_{11} + \frac{S_{12} S_{21} \Gamma_2}{1 - S_{22} \Gamma_2}}{1 - S_{22} \Gamma_2}$$

$$\Gamma_2 = \frac{Z_2 - Z_0}{Z_2 + Z_0}$$

4.20
(cont)

$$\text{Now: } \sqrt{Z_0} (a_1 + b_1) = \sqrt{Z_0} (a_1' + b_1')$$

$$\sqrt{Z_0} a_1 (1 + \Gamma_{11}) = \sqrt{Z_0} a_1' (1 + S_{11}') \quad (1)$$

$$\text{Also: } \sqrt{Z_0} (a_2 + b_2) = \sqrt{Z_0} b_2'$$

$$\sqrt{Z_0} b_2 (\Gamma_{22} + 1) = \sqrt{Z_0} b_2' \quad (2)$$

Taking the ratio of (2) to (1) leads to:

$$\frac{\sqrt{Z_0} b_2'}{\sqrt{Z_0} a_1' (1 + S_{11}')} = \frac{\sqrt{Z_0} b_2 (1 + \Gamma_{22})}{\sqrt{Z_0} a_1 (1 + \Gamma_{11})}$$

$$S_{11}' = \frac{b_2'}{a_1'} = \frac{\sqrt{Z_{01}}}{\sqrt{Z_{02}}} \frac{(1 + S_{11}') (1 + \Gamma_{22})}{(1 + \Gamma_{11})} \frac{b_2}{a_1}$$

$$S_{11}' = \frac{\sqrt{Z_{01}}}{\sqrt{Z_{02}}} \frac{(1 + S_{11}') (1 + \Gamma_{22})}{(1 + \Gamma_{11})} \frac{S_{21}}{1 - S_{22} \Gamma_{22}}$$

We can perform the same steps for terminating port (1) and then injecting the signal into port (2). In the mathematics, however, we just interchange the subscripts 1 and 2



$$S_{22}' = \frac{Z_0 (1 + \Gamma_{22}) - Z_{02} (1 - \Gamma_{22})}{Z_0 (1 + \Gamma_{22}) + Z_{02} (1 - \Gamma_{22})} \quad \text{where } \Gamma_{22} = S_{22} + \frac{S_{12} S_{21} \Gamma_1}{1 - S_{11} \Gamma_1}$$

$$\Gamma_1 = \frac{Z_{01} - Z_0}{Z_{01} + Z_0}$$

$$S_{12}' = \frac{\sqrt{Z_{02}}}{\sqrt{Z_{01}}} \frac{(1 + S_{22}') (1 + \Gamma_1)}{(1 + \Gamma_{22})} \frac{S_{12}}{1 - S_{11} \Gamma_1}$$

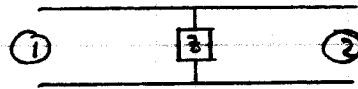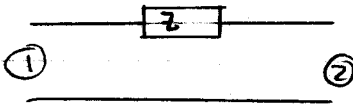4.28

Find the S-parameters. Show that $S_{12} = 1 - S_{11}$ for the series case, and $S_{12} = 1 + S_{11}$ for the shunt case. Assume a characteristic impedance of Z_0 .



Series: For S_{11} , terminate port 2 in Z_0 .

$$Z_{in} = Z + Z_0$$

$$S_{11} = \frac{Z + Z_0 - Z_0}{Z + Z_0 + Z_0} = \frac{Z}{Z + 2Z_0}$$

$$V_1 = \sqrt{Z_0} (a_1 + b_1) = \sqrt{Z_0} a_1 (1 + S_{11})$$

$$V_2 = \sqrt{Z_0} b_2$$

$$\text{But } \frac{V_2}{V_1} = \frac{Z_0}{Z + Z_0} = \frac{\sqrt{Z_0} b_2}{\sqrt{Z_0} a_1 (1 + S_{11})}$$

$$\begin{aligned} S_{11} = \frac{b_2}{a_1} &= \frac{(1 + S_{11}) Z_0}{Z + Z_0} = \left(1 + \frac{Z}{Z + 2Z_0}\right) \left(\frac{Z_0}{Z + Z_0}\right) = \frac{Z + 2Z_0 + Z}{Z + 2Z_0} \frac{Z_0}{Z + Z_0} \\ &= \frac{2(Z + Z_0)}{Z + 2Z_0} \frac{Z_0}{Z + Z_0} = \frac{2Z_0}{Z + 2Z_0} \end{aligned}$$

$$\text{So: } S_{11} = S_{22} = \frac{Z}{Z + 2Z_0}$$

$$S_{21} = S_{12} = \frac{2Z_0}{Z + 2Z_0}$$

$$\text{Note that } 1 - S_{11} = \frac{Z + 2Z_0 - Z}{Z + 2Z_0} = \frac{2Z_0}{Z + 2Z_0} = S_{12}$$

$$\text{Shunt: } Y_{in} = \frac{1}{Z} + \frac{1}{Z_0} = Y + Y_0$$


$$S_{11} = \frac{Y_0 - Y_{in}}{Y_0 + Y_{in}} = \frac{Y_0 - Y - Y_0}{Y_0 + Y + Y_0} = \frac{-Y}{Y + 2Y_0} = S_{22}$$

$$\left. \begin{aligned} V_1 &= \sqrt{Z_0} a_1 (1 + S_{11}) \\ V_2 &= \sqrt{Z_0} b_2 = V_1 \end{aligned} \right\} \Rightarrow \frac{b_2}{a_1 (1 + S_{11})} = 1$$


$$S_{21} = 1 + S_{11} = \frac{2Y_0}{Y + 2Y_0} = S_{12}$$

which also proves the requested relation.

Find the S parameters of This T network:

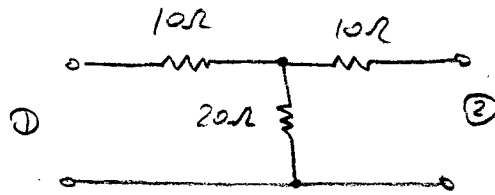

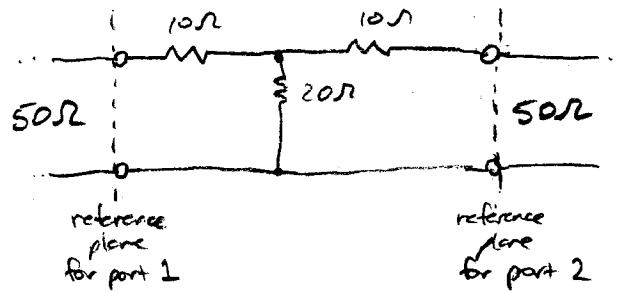Since the system impedance is not specified, we use 50Ω :




By symmetry, $S_{21} = S_{12}$ and $S_{11} = S_{22}$.

$$Z_{IN1} = 10\Omega + 20\Omega \parallel (10\Omega + 50\Omega) = 25$$

$$S_{11} = \Gamma_{in1} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{25 - 50}{25 + 50} = \underline{\underline{-\frac{1}{3}}}$$

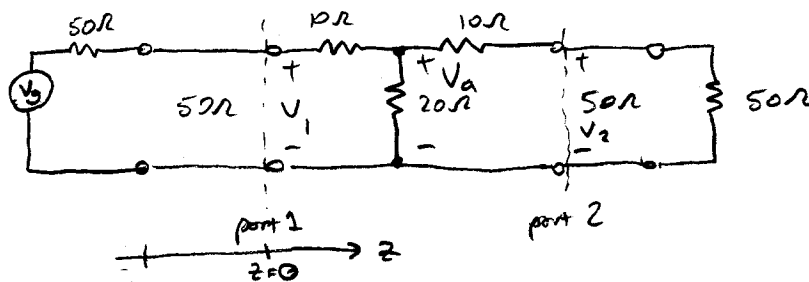To find S_{21} , apply a source to port 1 and match port 2:



On the "terminal" line connected to port 1,

$$V(z) = V_1^+ e^{-j\beta z} + V_1^- e^{j\beta z}$$

$$= V_1^+ e^{-j\beta z} + \Gamma_{in1} V_1^+ e^{j\beta z}$$

$$V(0) = V_1^+ (1 + \Gamma_{in1}) = V_1^+ (2/3) = V_1 \Rightarrow V_1^+ = \frac{3}{2} V_1$$

At port 2,

$$V_2 = V_2^- \quad (\text{since there is no reflected wave on the terminal line connected to port 2})$$

$$V_a = V_1 \cdot \frac{20 \parallel (10+50)}{10 + 20 \parallel (10+50)} = \frac{3}{5} V_1 \quad (\text{voltage divider})$$

$$V_2 = V_a \cdot \frac{50}{10+50} = \frac{5}{6} V_a \quad (\text{voltage divider})$$

$$\text{so, } V_2 = \frac{5}{6} \cdot \frac{3}{5} V_1 = \frac{1}{2} V_1$$


$$\text{and } S_{21} = \frac{V_2^-}{V_1^+} = \frac{V_2}{V_1^+} = \frac{1/2 V_1}{3/2 V_1} = \underline{\underline{\frac{1}{3}}}$$

$$\text{Thus, } \underline{\underline{S}} = \begin{bmatrix} -1/3 & 1/3 \\ 1/3 & -1/3 \end{bmatrix}$$

Another method

From p. 208, Pozar, the transmission matrix is
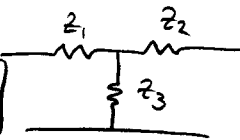
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + z_1/z_3 & z_1 + z_2 + z_1 z_2/z_3 \\ 1/z_3 & 1 + z_2/z_3 \end{bmatrix} = \begin{bmatrix} 3/2 & 25 \\ 1/20 & 3/2 \end{bmatrix}$$



From p. 211, the S parameters are

$$S_{11} = \frac{A + B/z_0 - Cz_0 - D}{A + B/z_0 + Cz_0 + D} = \frac{-2}{6} = \underline{\underline{-\frac{1}{3}}}$$

$$S_{21} = \frac{2}{A + B/z_0 + Cz_0 + D} = \frac{2}{6} = \underline{\underline{\frac{1}{3}}}$$