

ECEn 464 (Block 2)
Wireless Communication Circuits

Homework #5

Due Wednesday Dec. 4, 2013 in class

1. A transistor has S-parameters $S_{11} = .75\angle -120^\circ$, $S_{12} = .03\angle 40^\circ$, $S_{21} = 2.5\angle 80^\circ$, $S_{22} = .6\angle 70^\circ$.
 - (a) Find $G_{P,\max}$ in dB.
 - (b) Plot the gain circle for a power gain of half the maximum possible value.
 - (c) Find source network reflection coefficient Γ_s and the load network reflection coefficient Γ_L which achieve the gain value in part (b). Use a conjugate match at the input and the minimum magnitude reflection coefficient at the output.
 - (d) Draw stability circles for the source and load reflection coefficients and determine if the amplifier design is stable.
2. The equivalent temperature of a low noise amplifier is 50 K. A second stage amplifier has a noise figure of 2 dB. Both amplifiers have 15 dB gain and 1 dB compression points of 10 dBm, and the system bandwidth is 1 MHz. Following the amplifiers is a 100 foot length of coaxial cable with a 6 dB loss at the band center frequency (1 GHz). The output is connected to a detector that requires a signal at least 7 dB above the noise floor.
 - (a) Find the noise figure and equivalent noise temperature of this system.
 - (b) What is the input signal power in dBm that leads to an SNR of 7 dB at the output?
 - (c) What is the dynamic range of the system?
3. 12.16 [Amplifier gain and noise figure]
4. 12.17 [Amplifier gain and noise figure]
5. Consider the following circuit, where $R_{in} = -30(1 - A)\Omega$. Find the frequency of oscillation and the value of R_L that maximizes the delivered power.

