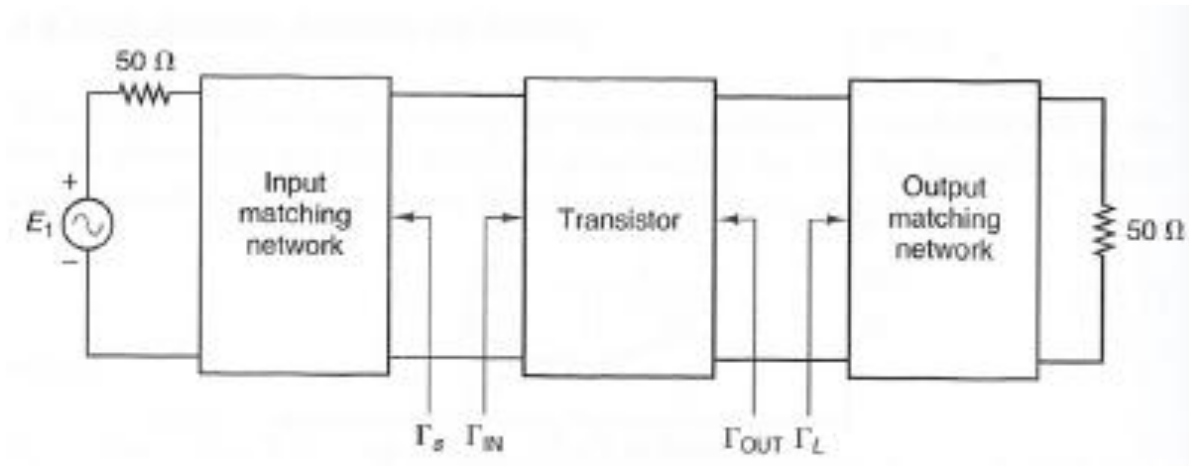


Bilateral design

$$S_{12} \neq 0$$



A conjugate match using transducer gain would require simultaneous adjustment of both input and output matching networks because changing one changes the other.

$$\Gamma_s^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s}$$

Design using power gain

- Using power gain allows us to decouple the input and output matching network designs

$$G_P = \frac{P_L}{P_{in}} = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

- We can write the input reflection coefficient in terms of the load reflection coefficient

$$|\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| = \left| \frac{S_{11} - S_{11}S_{22}\Gamma_L + S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| = \left| \frac{S_{11} - \Delta\Gamma_L}{1 - S_{22}\Gamma_L} \right|$$

- Then we can write the power gain in solely in terms of the load reflection coefficient

$$G_P = \frac{1}{1 - \left| \frac{S_{11} - \Delta\Gamma_L}{1 - S_{22}\Gamma_L} \right|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

Normalized power gain

-As before we will draw circles based on normalized gain

$$g_P = \frac{G_P}{|S_{21}|^2}$$

-We define a circle in terms of the location of its center and its radius in the Γ_L -plane.

$$\begin{aligned} C_P &= \frac{g_P(S_{22}^* - \Delta^* S_{11})}{1 + g_P(|S_{22}|^2 - |\Delta|^2)} \\ r_P &= \frac{[1 - 2k|S_{12}S_{21}|g_P + |S_{12}S_{21}|^2g_P^2]^{1/2}}{|1 + g_P(|S_{22}|^2 - |\Delta|^2)|} \\ k &= \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} \end{aligned}$$

Range of power gain


$$r_P = \frac{[1 - 2k|S_{12}S_{21}|g_P + |S_{12}S_{21}|^2g_P^2]^{1/2}}{|1 + g_P(|S_{22}|^2 - |\Delta|^2)|}$$

$$S_{11} = 0.641 \angle -171.3^\circ$$

$$S_{12} = 0.057 \angle 16.3^\circ$$

$$S_{21} = 2.058 \angle 28.5^\circ$$

$$S_{22} = 0.572 \angle -95.7^\circ$$

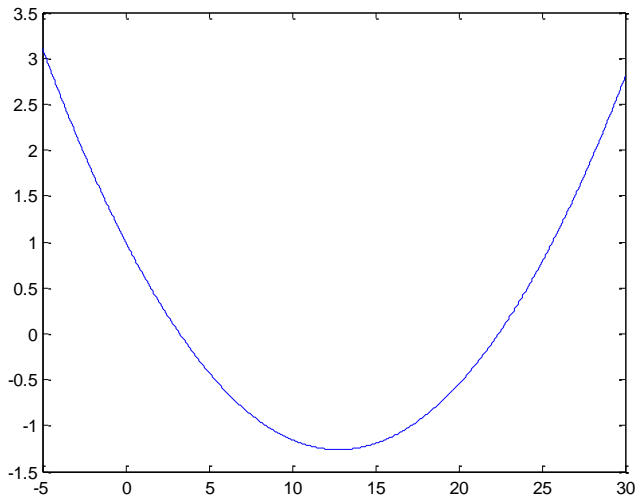


--Let's plot the numerator of the equation of the radius equation for actual values

--It is parabolic and has two zero crossings

--It is obvious that our radius can't be zero

Zoomed in range of normalized gain

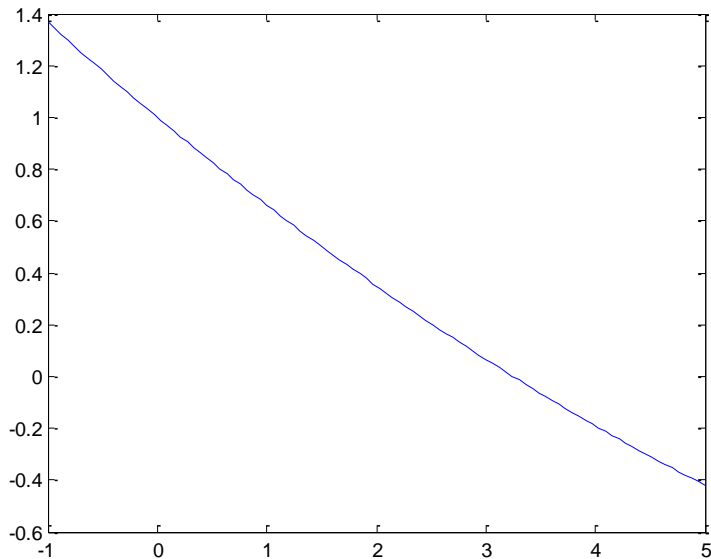

Radius must be positive so the maximum value of g_p is about 3.24.

Also if $g_p=0$ then the radius goes to 1 according to the equation

This means we can only choose g_p from 0 to 3.24 for this problem.

$$g_{P,\max} = \frac{1}{|S_{12}S_{21}|} [k - \sqrt{k^2 - 1}]$$
$$G_{P,\max} = \left| \frac{S_{21}}{S_{12}} \right| [k - \sqrt{k^2 - 1}]$$

Example problem

- Using S-parameters shown design an amplifier with a gain of 9 dB (7.94).
- Then we calculate where the center and radius
- Plot these on Smith Chart

$$S_{11} = 0.641 \angle -171.3^\circ$$

$$S_{12} = 0.057 \angle 16.3^\circ$$


$$S_{21} = 2.058 \angle 28.5^\circ$$

$$S_{22} = 0.572 \angle -95.7^\circ$$

$$g_p = \frac{G_p}{|S_{21}|^2} = \frac{7.94}{4.235} = 1.875$$

$$r_p = 0.431 \text{ and } C_p = 0.508 \angle 103.9^\circ$$

Smith Chart solution

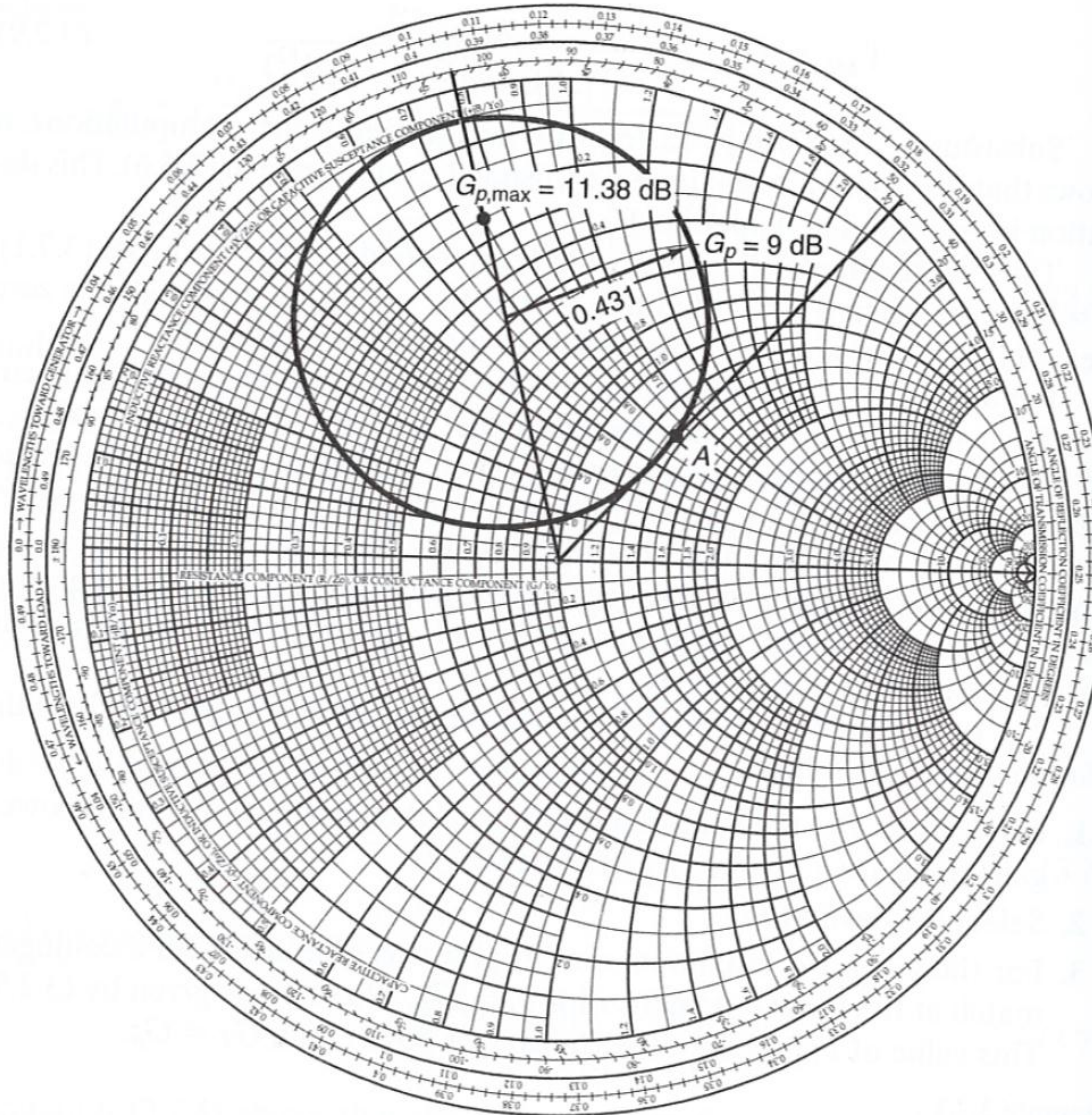

Get maximum output power

- Choose a Γ_L that lies on the circle, point A

$$\Gamma_L = 0.36 \angle 47.5^\circ$$

- Find corresponding Γ_s
- Because it is matched the source side VSWR unity

$$\begin{aligned} \Gamma_s^* &= S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \\ &= 0.629 \angle 175.51^\circ \end{aligned}$$

- The output VSWR is found as follows

$$|\Gamma_b| = \left| \frac{\Gamma_{\text{OUT}} - \Gamma_L^*}{1 - \Gamma_{\text{OUT}}\Gamma_L} \right| = \left| \frac{0.67 \angle -102.66^\circ - 0.36 \angle -47.5^\circ}{1 - 0.67 \angle -102.66^\circ (0.36 \angle 47.5^\circ)} \right| = 0.622$$

$$(\text{VSWR})_{\text{out}} = \frac{1 + 0.622}{1 - 0.622} = 4.3$$